

# *Proiect SCIA*



*Supervisor:*


Dr.Ing.Prof.Marius Neag  
Dr.Ing.Prof Onet Raul Ciprian

*Student:*


Morar Horea-Razvan  
Gr 2331
 
# 1. Project Thematic

The project aims to design and implement an analog interface that meets the specific requirements for use in analog signal processing applications. The interface consists of 4 blocks, connected in cascade, each with a specific role:



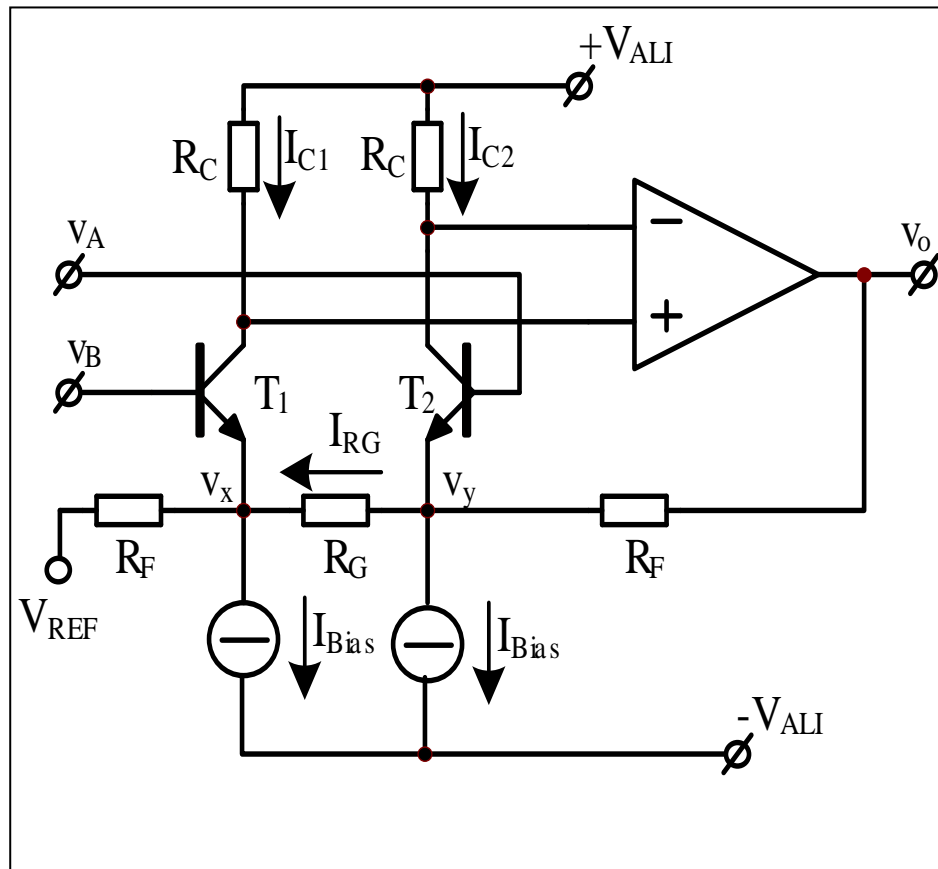
Given specifications: The first stage was configured as a passive current feedback instrumentation amplifier, with the following circuit:



And it has the following specifications:

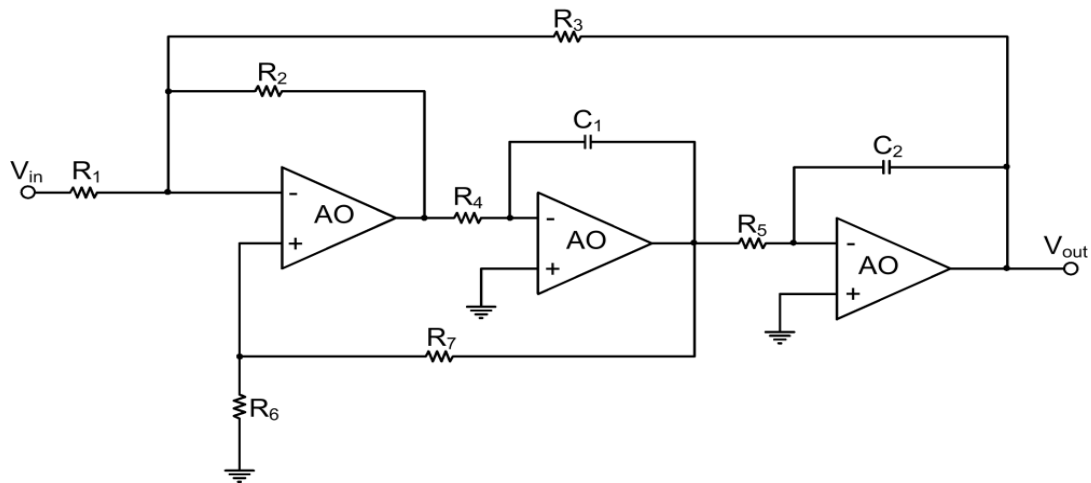1. Maximum amplitude (for minimum PGA gain):  $1.06\text{E-}01$
2. Minimum amplitude (for maximum PGA gain) :  $5.33\text{E-}02$
3. Unit of measurement : Voltage(differential)
4. Linear and modulus gain : 10


The second stage is a Analog Low-Pass Filter (KHN) with the following circuit:



And it had the given specifications:

1.  $|H_0|$  , linear gain in pass band :  $1.00\text{E+}00$
2. Minimum input resistance:  $1.00\text{E+}03$
3. Band : 6000 Hz
4. Quality factor, Q : 0.707

 
The third stage is a programmable gain amplifier with RG Parallel with the following circuit:



And it has the given specifications:

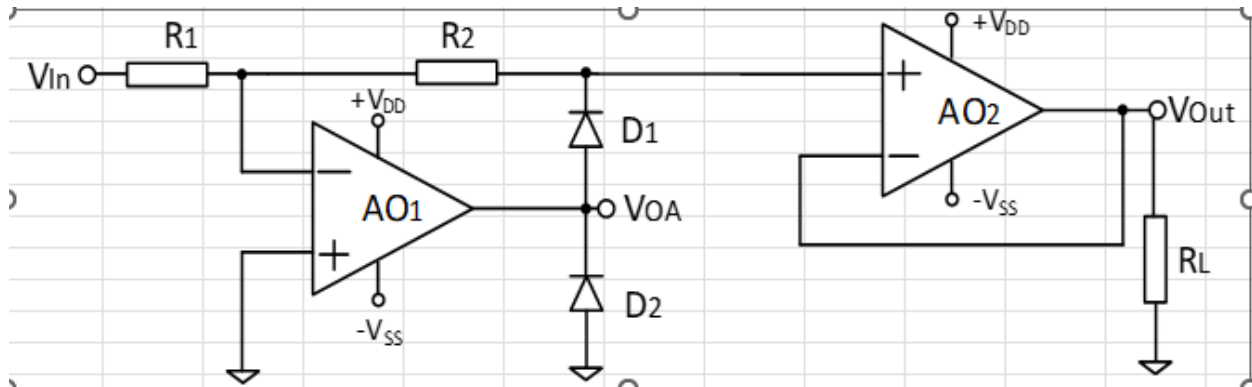1. Minimum gain in dBs : 9 dB
2. Resolution (minimum step) : 2 dB
3. Total number of steps : 4
4. Maximum gain in dBs : 1.50E+01

The fourth stage is a precision full-wave rectifier with the following circuit:



And it has the given specifications:

1. Gain (modulus and linear) : 1

## ***2.Sizing of Stages 1 / 2 / 3 / 4***

### ***2.1.Sizing of the first stage:***

Based on the following formula:

$$Av = \frac{Vo}{Vid} = \frac{Vo}{Va-Vb} = 1 + 2 * \frac{Rf}{Rg} \quad (1)$$

And the already known gain  $Av = 10$  results the following:

$$10 = 1 + 2 * \frac{Rf}{Rg} \quad (2)$$

$$9 = 2 * \frac{Rf}{Rg} \quad (3)$$

From which we get the following ratios of  $\frac{Rf}{Rg} = \frac{9k\Omega}{2k\Omega}$

And knowing this we could just select a value for the  $Rc$  resistances from the above circuit , which was 5k. This ensured us the necessary gain of 10.

### ***2.2.Sizing of the second stage:***

Dimensional parameters:

1. Resistors:

$$R1 = R2 = R3 = \dots = R7 = R \Rightarrow Ho = 1; \omega_0 = \frac{1}{R\sqrt{C1C2}}; Q = \frac{2}{3} \sqrt{\frac{C1}{C2}}$$

I chose  $R=15.9k \Omega$

2. Capacitors:

$$\omega_0 = 2\pi f_c = 2\pi 6000 = 37.680 \quad (1)$$

$$C_1 = \frac{3Q}{2\omega_0 R} = \frac{3*0.707}{2*37.680*15.9k} = 1.77nF \quad (2)$$

$$C_2 = \frac{4C_1}{9Q^2} = \frac{2}{3Q\omega_0 R} = \frac{2}{3*0.707*37.680*15.9k} = 1.57nF \quad (3)$$

### 2.3.Sizing of the third stage:

Resistors:

We choose Rf=10k

$$|A_v| = \{9dB, 11dB, 13dB, 15dB\} = \{2.82V, 3.55V, 4.47V, 5.62V\} \quad (1)$$

$$A_v = \frac{R_f}{R_g} \Rightarrow R_g = \frac{R_f}{A_v} \Rightarrow \quad (2)$$

$$\begin{cases} R_1 = 3.6k\Omega \\ R_2 = 2.82k\Omega \\ R_3 = 2.23k\Omega \\ R_4 = 1.8k\Omega \end{cases} \quad (4)$$

SW1	SW2	SW3	SW4	$R_f[\Omega]$	$R[\Omega]$	$A_v[dB]$	$A_v[\frac{V}{V}]$
VDD	0	0	0	10k	3.6k	9	2.82
0	VDD	0	0	10k	2.82k	11	3.55
0	0	VDD	0	10k	2.23k	13	4.47
0	0	0	VDD	10k	1.8k	15	5.62


## 2.4. Sizing of the fourth stage:

For the fourth stage we choose  $R=10k\Omega$  and we keep in mind the fact that the resistors need to be equal in order to get the gain 1.

# 3. Characterization of Stages 1 / 2 / 3 / 4

## 3.1. Characterization of Stage 1


DCOP Parameters:

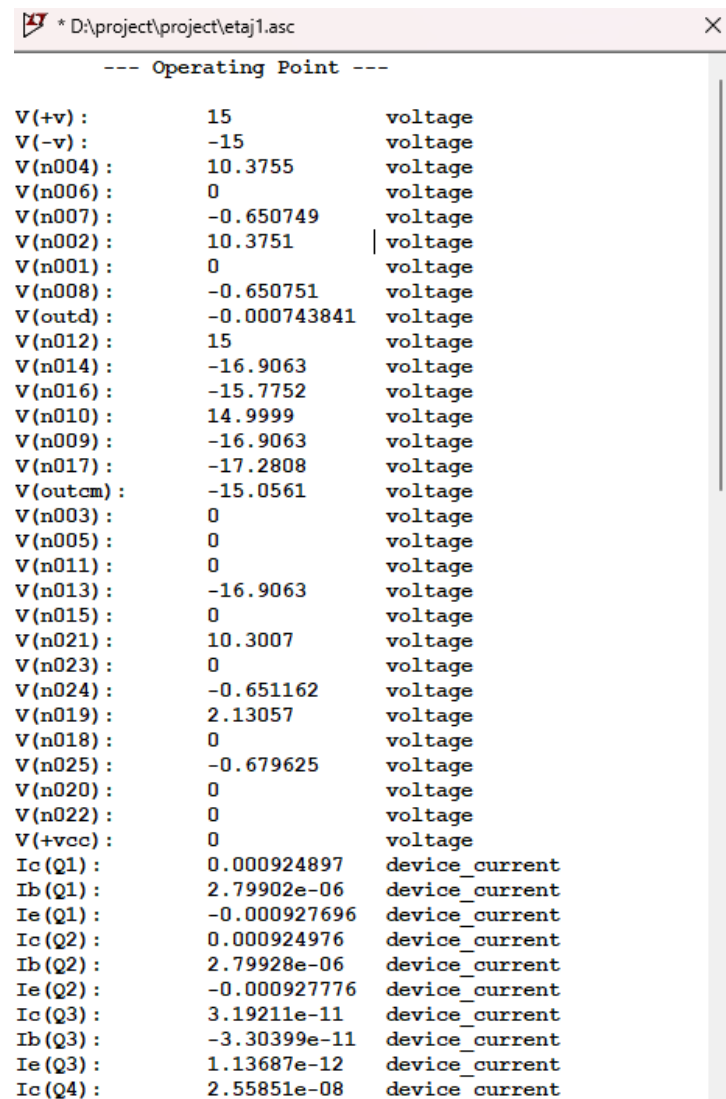

The screenshot shows a window titled "\* D:\project\project\etaj1.asc" with a close button. The content is a list of DCOP parameters organized into two sections: "voltage" and "device\_current".

--- Operating Point ---		
V(+v) :	15	voltage
V(-v) :	-15	voltage
V(n004) :	10.3755	voltage
V(n006) :	0	voltage
V(n007) :	-0.650749	voltage
V(n002) :	10.3751	voltage
V(n001) :	0	voltage
V(n008) :	-0.650751	voltage
V(outd) :	-0.000743841	voltage
V(n012) :	15	voltage
V(n014) :	-16.9063	voltage
V(n016) :	-15.7752	voltage
V(n010) :	14.9999	voltage
V(n009) :	-16.9063	voltage
V(n017) :	-17.2808	voltage
V(outcm) :	-15.0561	voltage
V(n003) :	0	voltage
V(n005) :	0	voltage
V(n011) :	0	voltage
V(n013) :	-16.9063	voltage
V(n015) :	0	voltage
V(n021) :	10.3007	voltage
V(n023) :	0	voltage
V(n024) :	-0.651162	voltage
V(n019) :	2.13057	voltage
V(n018) :	0	voltage
V(n025) :	-0.679625	voltage
V(n020) :	0	voltage
V(n022) :	0	voltage
V(+vcc) :	0	voltage
Ic(Q1) :	0.000924897	device_current
Ib(Q1) :	2.79902e-06	device_current
Ie(Q1) :	-0.000927696	device_current
Ic(Q2) :	0.000924976	device_current
Ib(Q2) :	2.79928e-06	device_current
Ie(Q2) :	-0.000927776	device_current
Ic(Q3) :	3.19211e-11	device_current
Ib(Q3) :	-3.30399e-11	device_current
Ie(Q3) :	1.13687e-12	device_current
Ic(Q4) :	2.55851e-08	device_current

 Demonstration of low frequency gain:  
Simulation used: .ac dec 100 .01 100Meg



Value obtained is 9.997 which approximately is 10 , which was the given spec.  
The spike is a overshoot because of the Opamp AD8065


Demonstration of band higher than that of filter  
Simulation used: .ac dec 100 .01 100Meg






Demonstration of CMRR,PSRR along with proper values.  
Simulation used: .ac dec 100 .01 100Meg

CMRR:

 


PSRR:

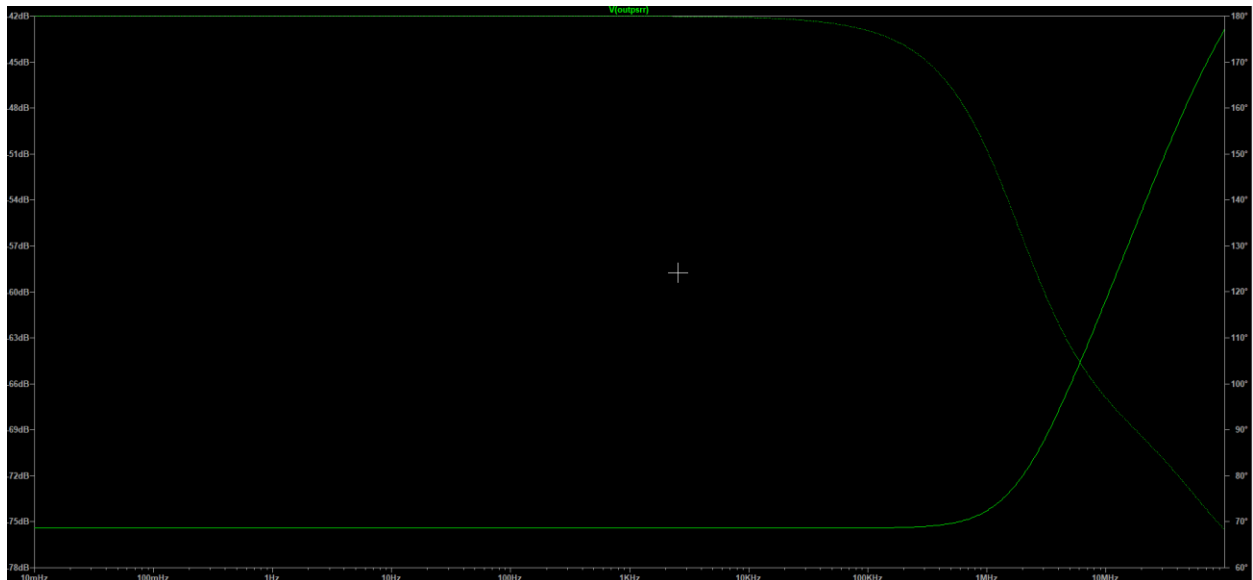

## Demonstration of linearity conditions

Simulation used: .tran 0 5m 0

 


## 3.2.Characterization of Stage 2

DCOP Parameters:


```
* D:\project\project\etaj2.asc
--- Operating Point ---

V(vcc):      15          voltage
V(vee):      -15         voltage
V(n001):     -0.000599986 voltage
V(n005):      0          voltage
V(n002):     -0.000400019 voltage
V(n003):     -0.000400002 voltage
V(n004):     -0.0004      voltage
V(vout_bpf): -0.000400016 voltage
V(vout_lpf): -0.00139996  voltage
V(n006):     -0.000199984 voltage
I(C1):       -2.52976e-29  device_current
I(C2):       -1.56993e-24  device_current
I(R1):       -3.7735e-08   device_current
I(R2):       1.25766e-08   device_current
I(R4):       1.0402e-12    device_current
I(R5):       1.03998e-12   device_current
I(R3):       -5.03126e-08  device_current
I(R6):       -1.25807e-08  device_current
I(R7):       1.25776e-08   device_current
I(Vcc):      -0.0192045    device_current
I(Vee):      0.0192046     device_current
I(V1):       -3.7735e-08   device_current
Ix(u1:100):  -3.04003e-12  subckt_current
Ix(u1:101):  -1.03997e-12  subckt_current
Ix(u1:102):  0.0064015     subckt_current
Ix(u1:103):  -0.00640157   subckt_current
Ix(u1:104):  5.03126e-08   subckt_current
Ix(u2:100):  -3.0398e-12   subckt_current
Ix(u2:101):  -1.04018e-12  subckt_current
Ix(u2:102):  0.0064015     subckt_current
Ix(u2:103):  -0.00640153   subckt_current
Ix(u2:104):  1.25817e-08   subckt_current
Ix(u3:100):  -3.05981e-12  subckt_current
Ix(u3:101):  -1.06013e-12  subckt_current
Ix(u3:102):  0.00640153    subckt_current
Ix(u3:103):  -0.0064015    subckt_current
Ix(u3:104):  -1.25755e-08  subckt_current
```

 
Demonstration of proper band  
Simulation used: .ac dec 100 1 10k



 Demonstration of GBW.  
Simulation used: .ac dec 100 1 10k



 Demonstration of linearity.  
Simulation used: .tran 0 5m 0



### 3.3.Characterization of Stage 3

#### DCOP Parameters:

```


--- Operating Point ---

I(in):      0      voltage
I(c1):      0      voltage
I(n004):    -1.12482e-06 voltage
I(out):     -0.00220569 voltage
I(n002):    -0.000399998 voltage
I(n003):    -0.000399998 voltage
I(n001):    -7.18703e-07 voltage
I(c2):      0      voltage
I(c3):      15      voltage
I(c4):      0      voltage
I(vcc):     15      voltage
I(vee):     -15      voltage
I(n005):    -1.43483e-06 voltage
I(R2):      3.98874e-10 device_current
I(Rf):      -1.80569e-07 device_current
I(R3):      1.79371e-07 device_current
I(R4):      3.9928e-10 device_current
I(R1):      3.98564e-10 device_current
I(S1):      -1.79371e-07 device_current
I(S2):      -3.9928e-10 device_current
I(S3):      -3.98874e-10 device_current
I(S4):      -3.98564e-10 device_current
I(Vin):     -1.80568e-07 device_current
I(Vo1):     0      device_current
I(Vo2):     0      device_current
I(Vo3):     0      device_current
I(Vo4):     0      device_current
I(Vcc):     -0.0064015 device_current
I(Vee):     0.0064017 device_current
Ix(u1:100): -3.04021e-12 subckt_current
Ix(u1:101): -1.0398e-12 subckt_current
Ix(u1:102): 0.0064015 subckt_current
Ix(u1:103): -0.0064017 subckt_current
Ix(u1:104): 1.80569e-07 subckt_current


```

Demonstration of all of the gain steps obtained.  
Simulation used: .ac dec 100 .01 100Meg


SW1:

 


SW2:

 

SW3:

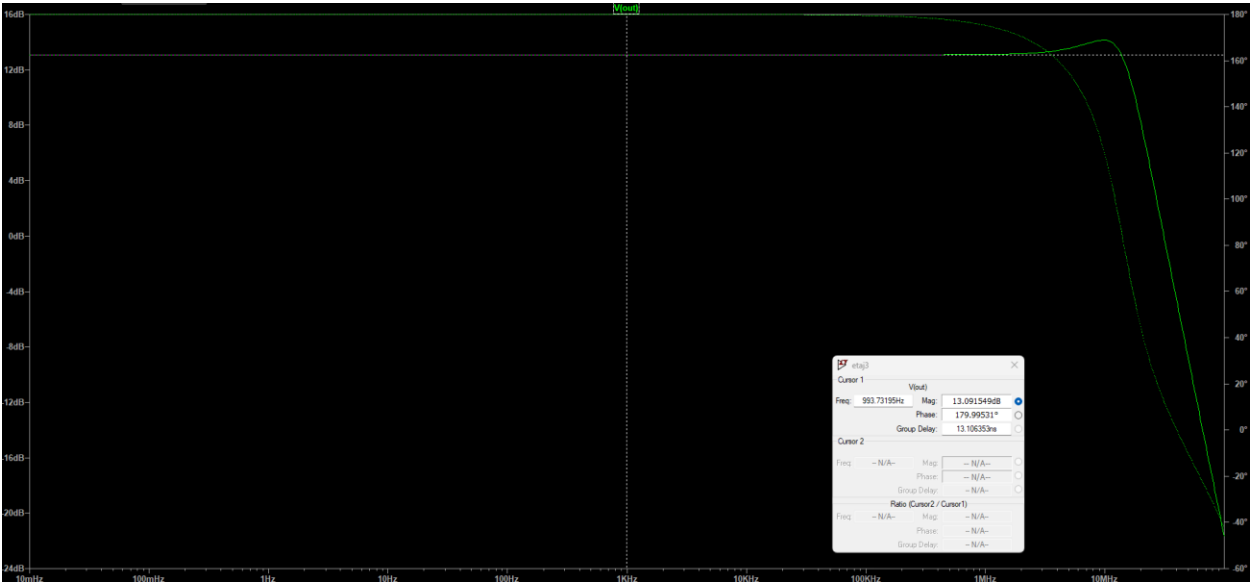

SW4:

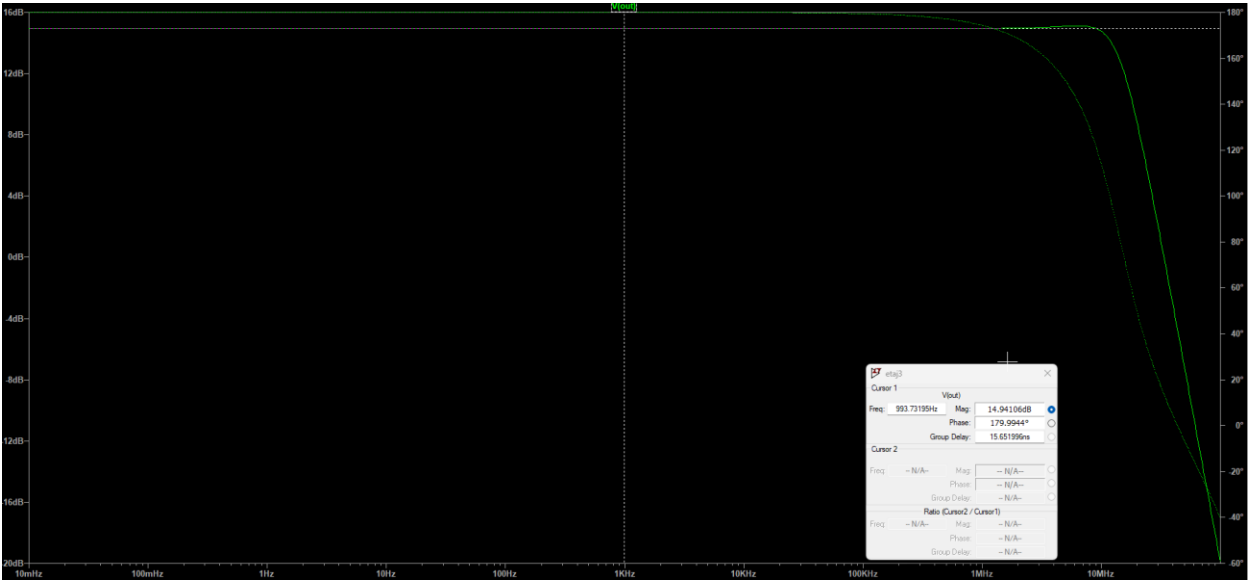

Demonstration off all band values for the gain steps.  
Simulation used: .ac dec 100 .01 100Meg

SW1:




SW2:






SW3:

 


SW4:

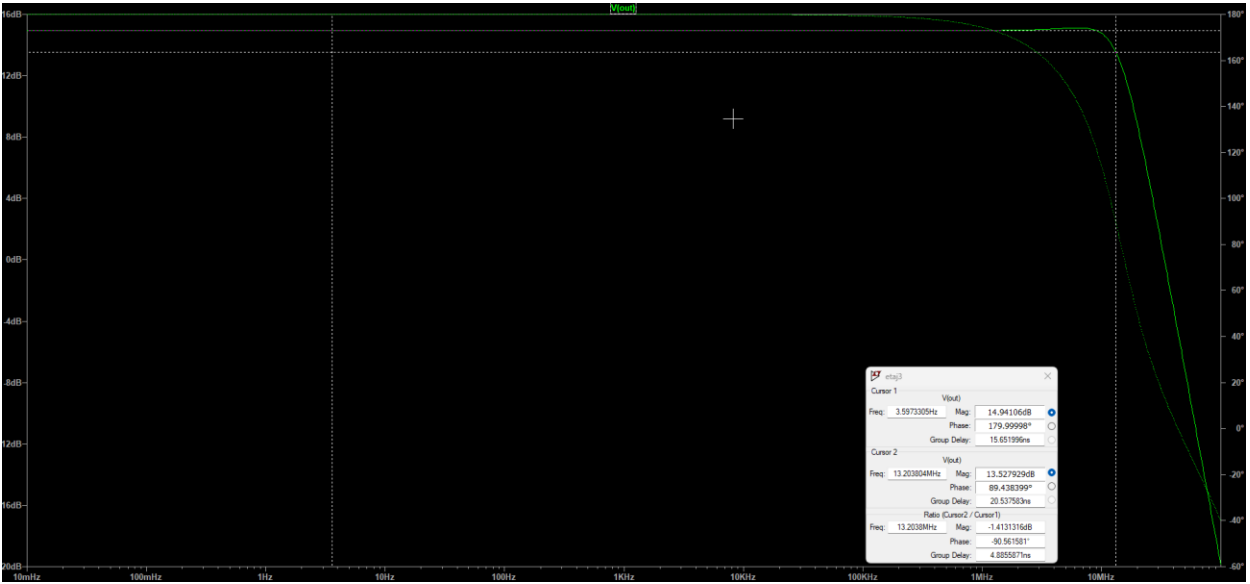

 
## Demonstration of THD and linearity

Simulation used: .tran 0 5m 0 50u

Linearity > specs for minimum gain and maximum input amplitude (for THD < 1%)




 Linearity > specs for maximum gain and minimum input amplitude (for THD < 1%)




### 3.4.Characterization of Stage 4

DCOP Parameters:

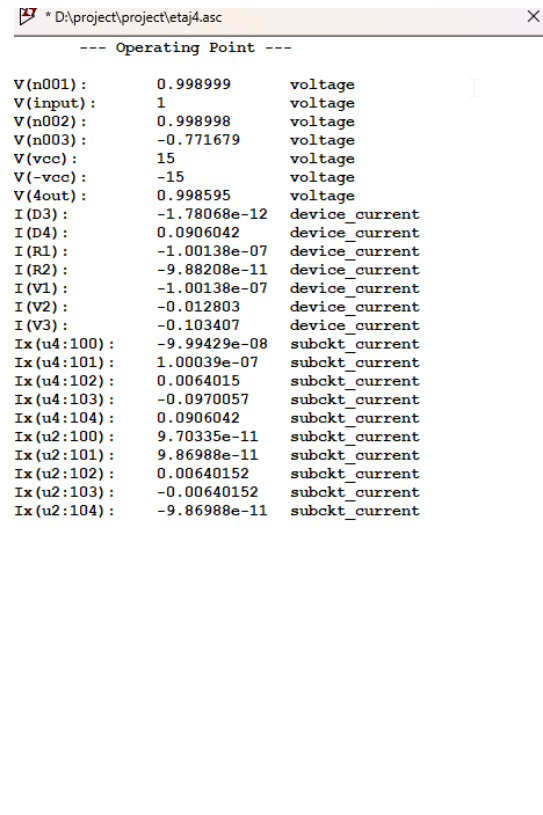



Demonstration of casting in DC sweep

Simulation used: .dc V1 -15 15 0.01

 


# Demonstration of implementing circuit functionality

Simulation used: .tran 0 5m 0 50u

  

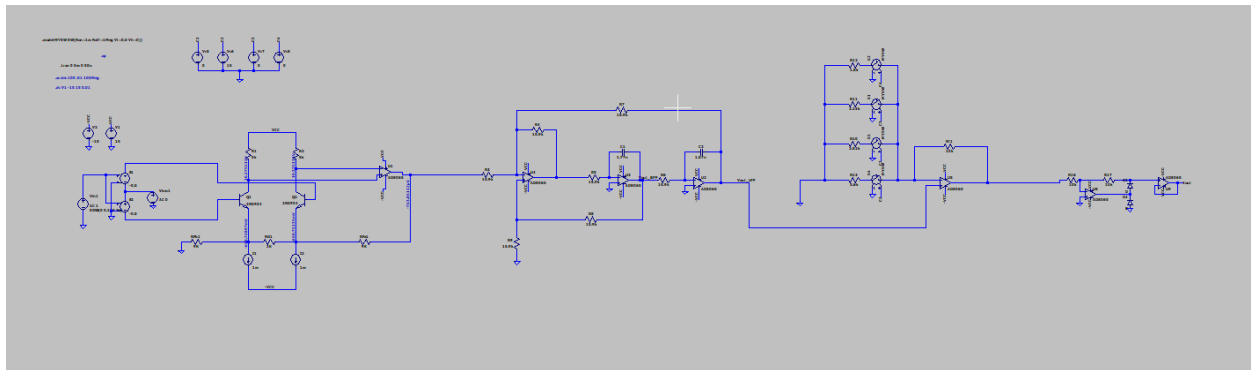
## 4. Validation and characterisation of the analog interface

The complete analog interface circuit is shown below. It integrates all the designed stages, including all the previously dimensioned components.



 Demonstration of .tran 0 5m 0 50u simulation:



## 5. Conclusion

	Specifications	Measurements
Gain  stage 1	10	9.997
H0  stage 2	1	1
Bandwidth stage 2	6000	6.016
Gain 1 stage 3	9dB	3.6
Gain 2 stage 3	11dB	2.82
Gain 3 stage 3	13dB	2.23
Gain 4 stage 3	15dB	1.8
Gain  stage 4	1	1

Following the measurements of each stage and comparing the results with the required specifications, there are no significant errors or differences, which indicates the correct functionality of the circuit within the required parameters.

The design, dimensioning, and characterization of the proposed analog interface have demonstrated the functionality of the circuit, according to the imposed requirements. The results obtained from the AC and Transient simulations confirm the correct operation of the circuit, validating the design parameters, namely gain, bandwidth, and linear range.